

Storage Elements

Basic Computational Model:

- So far we have discussed combinational components, i.e. the output is a function only of the current inputs
 - How do we “store” the values of variables for later use?

Sequential Components:

- In sequential components, the output is a function of the current inputs AND the current state of the circuit
- The current state is a function of a sequence of inputs over multiple time steps, starting from a known state.
 - The state is stored in storage elements:
(e.g. Latches, Flip-Flops, Registers, Memory)

Set/Reset Latch (S/R)


Symbol:



Truth Table:

	S	R	Q_t	Q_{t+1}	Q'_{t+1}
Keep{	0	0	0	0	1
	0	0	1	1	0
Reset{	0	1	0	0	1
	0	1	1	0	1
Set{	1	0	0	1	0
	1	0	1	1	0
Illegal{	1	1	0	?	?
	1	1	1	?	?

Gate-Level Implementation:

 

Notice that for the first time we allow “feedback”
between the combinational gates

Gated S/R Latch

Symbol:




Truth Table if E=1:

	S	R	Q_t	Q_{t+1}	Q'_{t+1}
Keep{	0	0	0	0	1
	0	0	1	1	0
Reset{	0	1	0	0	1
	0	1	1	0	1
Set{	1	0	0	1	0
	1	0	1	1	0
Illegal{	1	1	0	?	?
	1	1	1	?	?

Truth Table if E=0:

IF $Q_t=1$,
 $Q_{t+1}=1$ and $Q'_{t+1}=0$
 IF $Q_t=0$,
 $Q_{t+1}=0$ and $Q'_{t+1}=1$ ₃

Gate-Level Implementation:

 

D-Latch

Avoiding the “illegal combinations”:

Force S and R to be always different

Symbol:




Truth Table:

	E	D	Q_t	Q_{t+1}	Q'_{t+1}
Keep	0	0	0	0	1
	0	0	1	1	0
	0	1	0	0	1
	0	1	1	1	0
Read	1	0	0	0	1
	1	0	1	0	1
	1	1	0	1	0
	1	1	1	1	0

D stands for “Data”!!!

D-Latch provides basic memory capability

Gate-Level Implementation:

 

Introducing the “Clock”

Asynchronous vs. Synchronous Design:

- Signals may take different paths in the design and arrive at any arbitrary time and order
 - The Latches that we examined will respond immediately to any signal change at their inputs, so the result may depend on the time and order of signal arrival
 - This makes our circuit unpredictable
- How do we synchronize the computation ?

Clock:

A periodic signal that imposes a synchronization point



D Flip-Flop Master/Slave


Basic Idea:

Connect two latches in series, the “Master” and the “Slave”. Use a clock signal to enable the Slave and the inverse of the clock signal to enable the Master. The Master stores the result while the clock is 0 and then passes it to the Slave when the clock is 1.

Symbol:



Implementation:

 

D Flip- Flop with Enable


Operation:

E	Function	Comment
0	$Q_{t+1} = Q_t$	Keep Previous Value
1	$Q_{t+1} = In_t$	Load Input Data

Symbol:



Implementation:

 


Note: The MUX Passes the In to the D when E=1 and the Q to the D when E=0

D Flip- Flop with Enable and Clear


Operation:

C	E	Function	Comment
0	0	$Q_{t+1}=Q_t$	Keep Previous Value
0	1	$Q_{t+1}=In_t$	Load Input Data
1	0	$Q_{t+1}=0$	Clear to 0
1	1	$Q_{t+1}=0$	Clear to 0


Symbol:

 

Implementation:

 


8-Bit Register with Enable and Clear

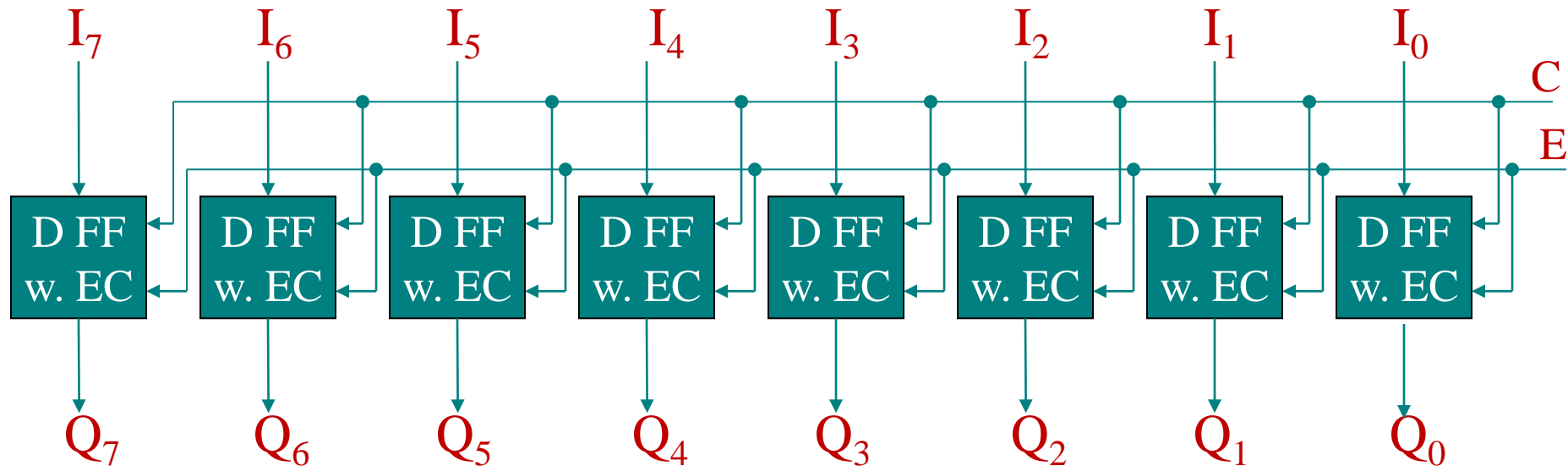

Note: The same Enable E and Clear C signals are used to drive all D Flip-Flops so that they all Clear, Load from the inputs $I[7:0]$, or Keep the previous Values $Q[7:0]$
(The clock signals are not shown for clarity of the figure)

Register-Based Circuit

Block Diagram:

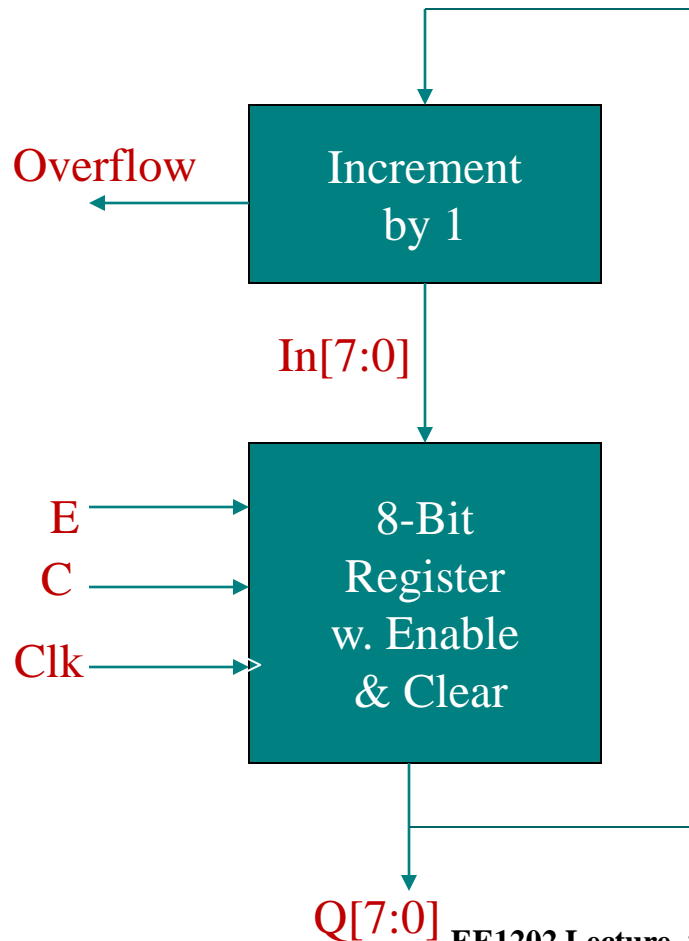

Operation:


- Initialize the Register to “00000000” by C=1 and sending a clock pulse
- Take the current value of the Register, Q[7:0], increment it by “1” and store it back into the Register by C=0, E =1, and sending a clock pulse

It's a counter!!!

- Overflow asserted when counter “wraps around”

Building an increment by “1” Circuit

Simple Idea – Use an Adder:

 

Hardware Reduction:

$$s_i = x_i \oplus y_i \oplus c_i \text{ but } x_i = 0, \text{ so } s_i = 0 \oplus y_i \oplus c_i \Rightarrow \mathbf{s_i = y_i \oplus c_i}$$


$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i \oplus y_i) \text{ but } x_i = 0, \text{ so } c_{i+1} = 0 \cdot y_i + c_i \cdot (0 \oplus y_i) \Rightarrow \mathbf{c_{i+1} = c_i \cdot y_i}$$

$$\text{Special Case: } s_0 = c_{in} \oplus y_0 \Rightarrow s_0 = 1 \oplus y_0 \Rightarrow \mathbf{s_0 = y_0'}$$

$$\text{and } c_1 = c_{in} \cdot y_0 \Rightarrow c_1 = 1 \cdot y_0 \Rightarrow \mathbf{c_1 = y_0}$$


Reduced Hardware Implementation

Full Adder Reduces to Half Adder:

 

8-Bit increment Circuit

Hierarchical Implementation:

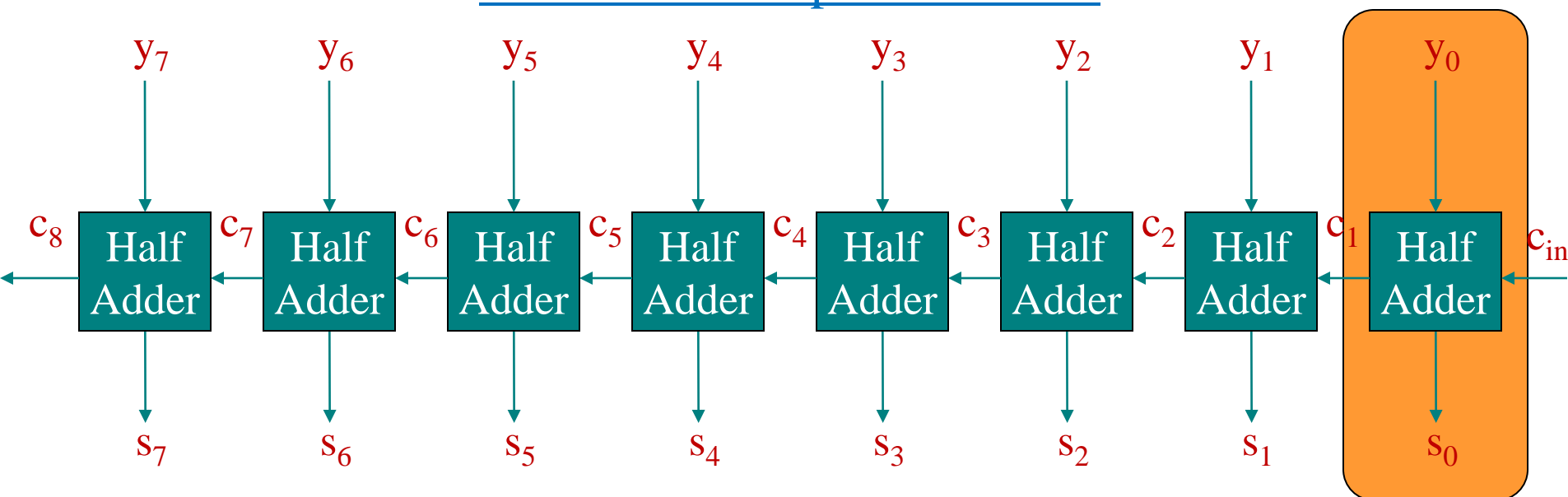

Special Case: $s_0 = c_{in} \oplus y_0 \Rightarrow s_0 = 1 \oplus y_0 \Rightarrow s_0 = y_0'$

and $c_1 = c_{in} \cdot y_0 \Rightarrow c_1 = 1 \cdot y_0 \Rightarrow c_1 = y_0$




8-Bit Counter with Load, Count and Reset

Operation:


Reset	Count	Load	Operation
0	0	0	Keep Previous
0	0	1	Load from IN
0	1	0	Count Up by 1
0	1	1	Load from IN
1	0	0	Reset to 0
1	0	1	Reset to 0
1	1	0	Reset to 0
1	1	1	Reset to 0

Symbol:

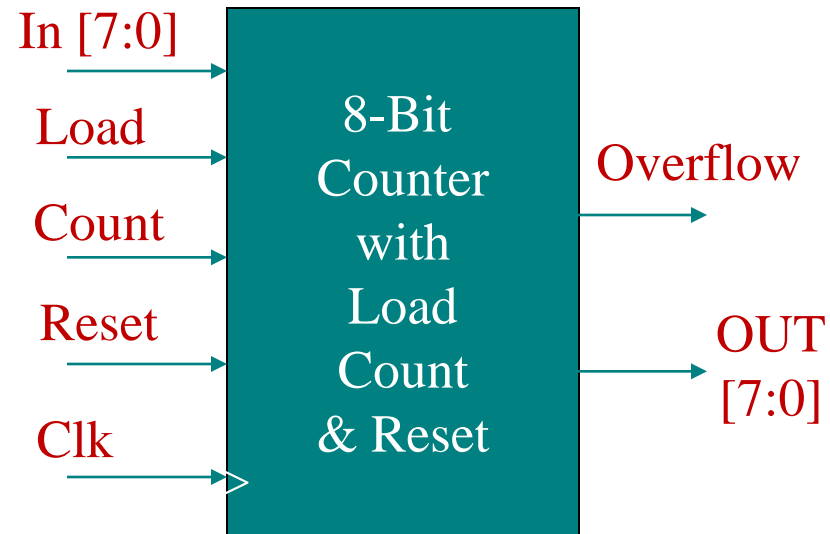

8-Bit Counter with Load, Count and Reset

Block Diagram:

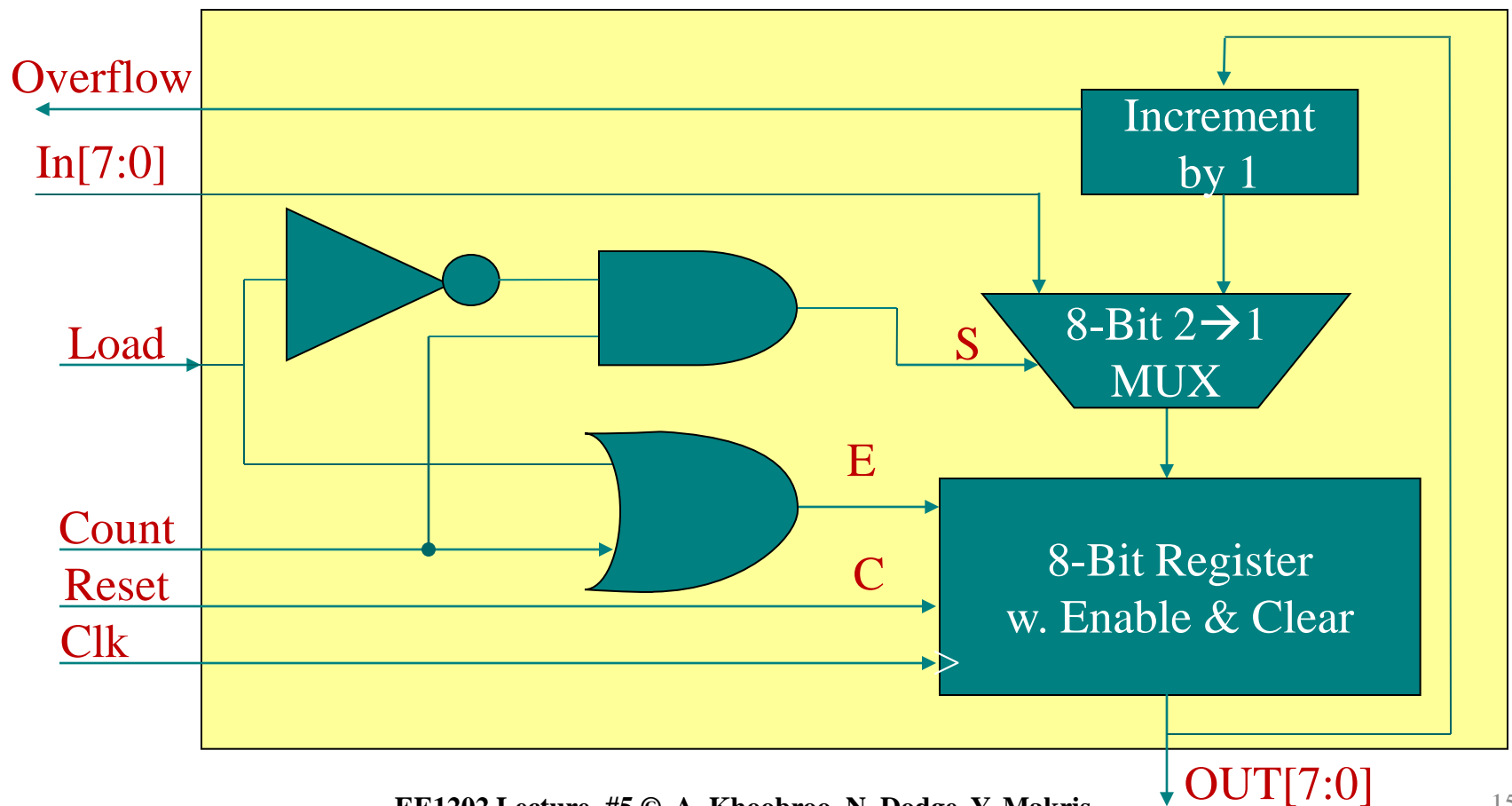


AC RL and RC Circuits

- When a sinusoidal AC voltage is applied to an RL or RC circuit, the relationship between voltage and current is altered.
- The voltage and current still have the same frequency and cosine-wave shape, but voltage and current no longer rise and fall together.
- To solve for currents in AC RL/RC circuits, we need some additional mathematical tools:
 - Using the complex plane in problem solutions.
 - Using transforms to solve for AC sinusoidal currents.


Imaginary Numbers

- Solutions to science and engineering problems often involve $\sqrt{-1}$.
- Scientists define $i = -\sqrt{-1}$.
- As we EE's use i for AC current, we define $j = +\sqrt{-1}$.
- Thus technically, $j = -i$, but that does not affect the math.
- Solutions that involve j are said to use “imaginary numbers.”
- Imaginary numbers can be envisioned as existing with real numbers in a two-dimensional plane called the “Complex Plane.”

 


Complex Plane

 - In the complex plane, imaginary numbers lie on the y-axis, real numbers on the x-axis, and complex numbers (mixed real and imaginary) lie off-axis.
- For example, 4 is on the +x axis, -8 is on the $-x$ axis, $j6$ is on the +y axis, and $-j14$ is on the $-y$ axis.
- Complex numbers like $6+j4$, or $-12-j3$ lie off-axis, the first in the first quadrant, and the second in the third quadrant.




Transformation

 

- Transforms move a problem from the real-world domain, where it is hard to solve, to an alternate domain where the solution is easier.
- Sinusoidal AC problems involving R - L - C circuits are hard to solve in the “real” time domain but easier to solve in the ω -domain.

The ω Domain

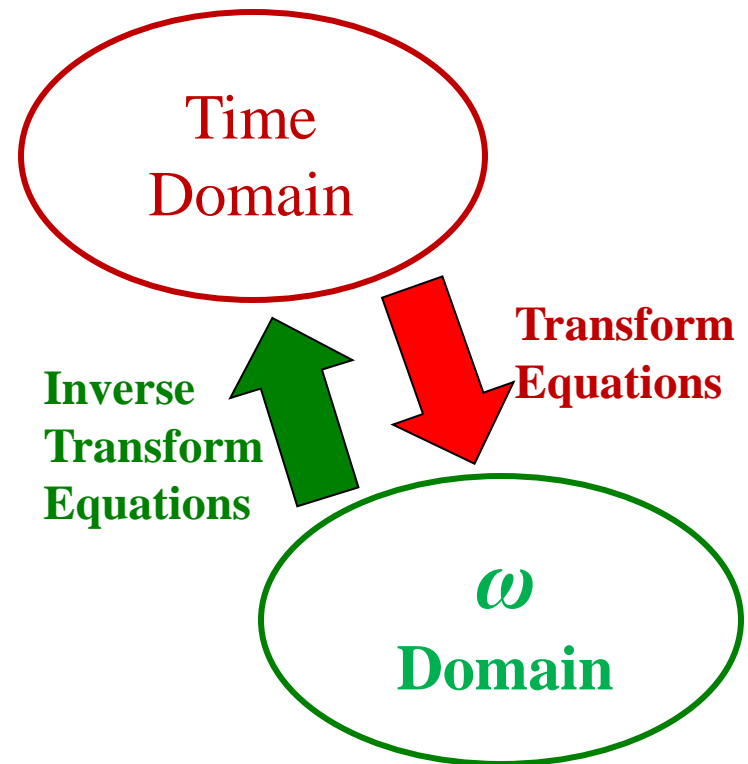- In the time domain, *RLC* circuit problems must be solved using calculus.
- However, by transforming them to the ω domain (a radian frequency domain, $\omega = 2\pi f$), the problems become algebra problems.
- A catch: We need transforms to get the problem to the ω domain, and inverse transforms to get the solutions back to the time domain!



Euler's formula

- You should remember Euler's formula from trigonometry (if not, get out your old trig textbook and review):
- The alternate expression for $e^{\pm jx}$ is a complex number. The real part is $\cos x$ and the imaginary part is $\pm j\sin x$.
- We can say that $\cos x = \text{Re}\{e^{\pm jx}\}$ and $\pm j\sin x = \text{Im}\{e^{\pm jx}\}$, where Re = "real part" and Im = "imaginary part."
- We usually express AC voltage as a cosine function. That is, an AC voltage $v(t)$ can be expressed as $v(t) = V_p \cos \omega t$, where V_p is the peak AC voltage.
- Therefore we can say that $v(t) = V_p \cos \omega t = V_p \text{Re}\{e^{\pm j\omega t}\}$. This relation is important in developing inverse transforms.

Frequency Domain Transformation

Element	Time Domain	ω Domain Transform
AC Voltage	$V_p \cos \omega t$	V_p
Resistance	R	R
Inductance	L	$j\omega L$
Capacitance	C	$1/j\omega C$

- The time-domain, sinusoidal AC voltage is normally represented as a cosine function, as shown above.
- R , L and C are in Ohms, Henrys and Farads.
- Skipping some long derivations (which you will get in EE 3301), transforms for the ω domain are shown above.
- Notice that the AC voltage ω -transform has no frequency information. However, frequency information is carried in the L and C transforms.

Frequency Domain Transformation

Element	Time Domain	ω Domain Transform
AC Voltage	$V_p \cos \omega t$	V_p
Resistance	R	R
Inductance	L	$j\omega L$
Capacitance	C	$1/j\omega C$

- Because we are studying constant-frequency sinusoidal AC circuits, the ω -domain transforms are constants.
- This is a considerable advantage over the time-domain situation, where t varies constantly (which is why solving for sinusoidal currents in the time domain is a calculus problem).
- Two other items:
 - In the ω -domain, the units of R , $j\omega L$, and $1/j\omega C$ are Ohms.
 - In the ω -domain, Ohm's Law and Kirchoff's voltage and current laws still hold.