

# Adder Implementation

Addition of binary digits

$x_i + y_i + c_i$			$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = x_i' \cdot y_i' \cdot c_i + x_i' \cdot y_i \cdot c_i' + x_i \cdot y_i' \cdot c_i' + x_i \cdot y_i \cdot c_i =$$

=... (Algebraic Manipulation)...

$$= x_i \oplus y_i \oplus c_i$$

(Intuitively, when one input bit is 1, or when all three are 1, then  $s_i=1$ )

$$C_{i+1} = x_i' \cdot y_i \cdot c_i + x_i \cdot y_i' \cdot c_i + x_i \cdot y_i \cdot c_i' + x_i \cdot y_i \cdot c_i =$$


=... (Algebraic Manipulation)...

$$= x_i \cdot y_i + c_i \cdot (x_i \oplus y_i)$$

(Intuitively, when two input bits are 1, or when all three are 1, then  $c_{i+1}=1$ )

# Full Adder


Symbol:

 

$$s_i = x_i \oplus y_i \oplus c_i$$


$$c_{i+1} = x_i \cdot y_i + c_i \cdot (x_i \oplus y_i)$$

Gate-Level Implementation:

 


# 8-Bit Ripple Carry Adder

## Hierarchical Implementation:

 

# Full Subtractor

Subtraction of binary digits

 


$x_i - y_i - b_i$			$b_{i+1}$	$d_i$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$d_i = (x_i \odot y_i) \odot b_i$$

$$b_{i+1} = (x_i \odot y_i) \cdot b_i + x_i' \cdot y_i$$

# 8-Bit Ripple Borrow Subtractor

## Hierarchical Implementation:

 

# 2's Complement Representation

## Obtaining 2s Complement of a Binary Number:

Invert All Bits, Add 1 to the Result, Ignore MSB Carry

### Example:

A=01001010

Invert all Bits: A'=10110101

Add 1:  $10110101 + 00000001 = 10110110$

### The 2's Complement of 0 is itself:

B=00000000

Invert all Bits: B'=11111111

Add 1:  $11111111 + 00000001 = 1\ 00000000$

Ignore the MSB Carry: 00000000

Note: The 2's complement of the 2's complement of a number is the number itself

# Subtraction by 2's Complement Addition

## Alternative Subtraction Method:

(A-B: A is the “Minuend”, B is the “Subtrahend”)

The difference A-B can be obtained by:

- i) taking the 2's complement of the subtrahend, and
- ii) adding it to the minuend, ignoring any MSB carry

### Example:

$$A = 11001010 = (202)_{10}, B = 00110110 = (54)_{10}$$

i) 2's Complement of B is :

$$B' + 1 = 11001001 + 00000001 = 11001010$$

ii) Adding it to A gives:

$$11001010 + 11001010 = 1\ 10010100 = (148)_{10}$$


(Ignoring the MSB carry of the addition)

Note: We restrict ourselves to positive integers with  $A > B$

# 8-bit Adder/Subtractor

## Operation:

S	Function	Comment
0	$F=X+Y$	Addition
1	$F=X+Y'+1$	Subtraction

 


## Explanation:

When  $S=0$ , the circuit behaves as an 8-bit adder, while when  $S=1$ , it behaves as an 8-bit subtractor. Subtraction is performed by adding the 2's complement of  $Y$ . The 2's complement of  $Y$  is obtained by inverting each bit of  $Y$ , which gives us  $Y'$ , and then adding 1 to it



# 8-bit Adder/Subtractor

## Hierarchical Implementation:

 

Note: The XOR gates behave as inverters when  $S=1$ , and the 1 for obtaining the 2's complement is added by connecting  $S$  to the carry  $c_0$

# 2 to 1 Multiplexer (Selector)

## Operation:


S	Function	Comment
0	$F=A$	Select A
1	$F=B$	Select B

S	A	B	S'	$S' \cdot A$	$S \cdot B$	F
0	0	0	1	0	0	0
0	0	1	1	0	0	0
0	1	0	1	1	0	1
0	1	1	1	1	0	1
1	0	0	0	0	0	0
1	0	1	0	0	1	1
1	1	0	0	0	0	0
1	1	1	0	0	1	1


## Logic Expression:

$$F=(S' \cdot A)+(S \cdot B)$$


## Symbol:

 

## Gate-Level Implementation:

 

## 8-Bit 2 to 1 Mutliplexer

 

**Note:** The same select signal  $S$  is used to drive all MUXs so that ALL the bits of either  $A$  or  $B$  pass through


# 4 to 1 Multiplexer (Selector)

## Operation:

$S_1S_0$	Function	Comment
00	$F=A$	Select A
01	$F=B$	Select B
10	$F=C$	Select C
11	$F=D$	Select D
 
## Logic Expression:

$$F=(S_1' \cdot S_0' \cdot A)+(S_1' \cdot S_0 \cdot B)+ \\ (S_1 \cdot S_0' \cdot C)+(S_1 \cdot S_0 \cdot D)$$



# Decision Making

## Generating Decision Signals:


So far we have built components that manipulate binary numbers of a given width and produce a result of the same width, such as addition, subtraction, & propagation.

How do we generate single-bit signals, such as the S signal of the MUX ?


## Example:

$S=1$  if and only if  $A[7:0] = 00000000$

## Symbol:

 

## Implementation:

 

# Signal Propagation Through Gates

## Physical Signal Implementation:

- We learned how to design circuits based on the abstract notation of “logic 1” and “logic 0”
- These two values are physically implemented using two distinct levels of voltage, e.g. 0 V for “0” and 5 V for “1” (also called “low” and “high” voltage)

## Signal Transitions:


- A signal remains at a voltage level to represent 0 or 1
- Transition from high to low or from low to high signifies a change in the logic value from 1 to 0 or 0 to 1

## Propagation Delay:

- The time that it takes for a logic gate to generate the output value based on the input values


# Timing Diagrams

## Symbolic Representation:

 


AND  
 $C = A \cdot B$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 

## Timing Diagrams (cont'd)

Actual  
Timing:

 

$$t_p = (t_{PLH} + t_{PHL}) / 2$$